

Operational Amplifiers

Tuesday, 20 January 2026 09:51


Definitions

→ Loading Effect

- Effect of a load on a signal
- Distorts incoming signal
- The lower the resistance, the higher the loading effect
- The higher the current drawn, the higher the loading effect

→ Input Impedance

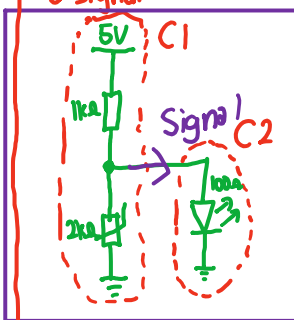- Impedance is the resistance 'seen' by a signal




In this case, the LED Resistance is C2's input impedance (100Ω)

→ Higher input impedance is Better!

- Lower Distortion by previous stage
- Reduce loading effect

→ Output impedance

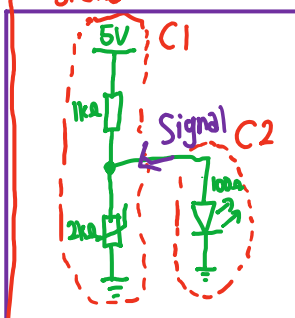- The resistance seen by an incoming signal




In this case, C1's output impedance is $1k\Omega + 2k\Omega = 3k\Omega$

→ Lower Output Impedance is better!

- Reduce distortion by next stage
- Able to supply higher current to next stage


Not in Syllabus

Simplified explanation of impedance

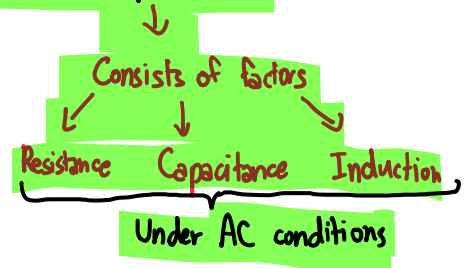

Amplifiers

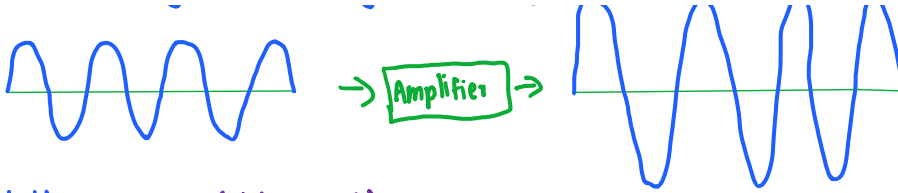→ Increases magnitude of Signal's Voltage/Current/Power



→ Voltage Gain (No unit)

↳ A_V , the increase of the $\frac{V_{out}}{V_{in}}$

↳ $A_V = \frac{V_{out}}{V_{in}}$

→ Uses

↳ When small signals need to be made bigger

↳ Audio-amp

↳ Heartbeat monitor

Op-Amp


→ Has High Input Impedance (in $M\Omega$)

↳ Draws low current

↳ Very low loading effect

→ Negligible Output Impedance

→ Symbol

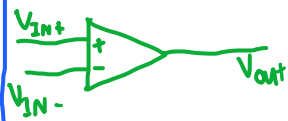

V_{IN+}	Non-Inverting Input
V_{IN-}	Inverting Input
V_{out}	Output


→ Amplification

↳ Amplifies The difference between V_{IN+} and V_{IN-}

↳ Has limit of $V_{CC} - 1.5V$ ✱ Even if A_{OL} is higher!

→ Configurations


↳ Open Loop

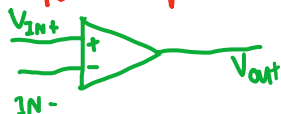

A_{OL}	Open loop gain
----------	----------------

✱ Rarely Used. A_{OL} is too High → Stuck at HIGH or LOW

↳ Closed Loop


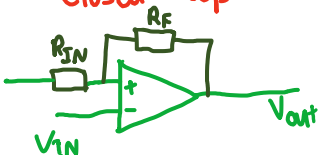


A_{CL}	Closed Loop Gain
R_{IN}	Resistor at input
R_F	Feedback Resistor

→ Types

↳ Non-Inverting Amplifier



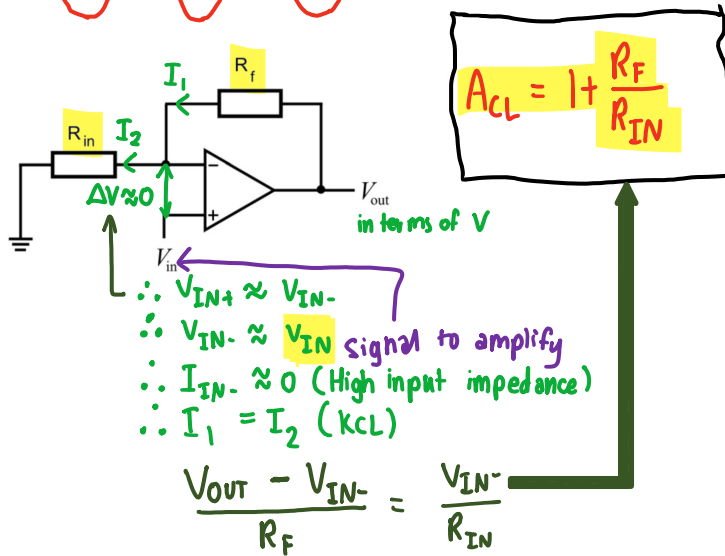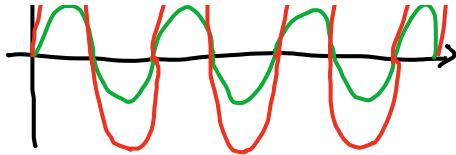

Voltage Follower

- Has ideal A_{CL} of 1
 - ↳ Input voltage = Output voltage
- ↑↑ Input impedance
 - ↳ ↓↓ Loading effect
- ↓↓ Output impedance

